

1번.

entity NEW_GATE is

port (A, B,C,D : in bit; Y: out bit); --input A,B,C,D output Y

end;

architecture NEW_GATE of NEW_GATE is --architecture에서 NEW_GATE 내부회로서술

begin

Y<= ((A OR B)NOR(C NAND D)); --output Y의 연산

end;

entity tb_NEW_GATE is --테스트벤치 entity선언

port (Y : out bit) ;

end tb_NEW_GATE ;

architecture simulation of tb_NEW_GATE is --tb achitecture 선언

component NEW_GATE --component 선언

port (A, B,C,D: in bit; Y : out bit);

end component;

signal a,b,c,d : bit; --signal 선언

begin

a <= '0', '1' after 20 ns, '0' after 40 ns; --파형 생성문으로 입력 신호 생성


b <= '0', '1' after 10 ns, '0' after 20 ns, '1' after 30 ns, '0' after 40 ns;

c <= '0', '1' after 40 ns, '0' after 80 ns;

d <= '0', '1' after 20 ns, '0' after 40 ns, '1' after 60 ns, '0' after 80 ns;

U0 : NEW_GATE port map (A=>a, B=>b,C=>c,D=>d,Y=>Y); --component 실체화

end ;

 

출력 Y가 1이 되기 위한 입력 신호의 조건

NOR게이트의 출력이 1이 되어야 하기 때문에 NOR게이트의 입력이 0,0이 되어야 한다.

따라서, (A OR B)가 0이면서 (C NAND D)가 0이어야 하기 때문에

위에 그림처럼 A=0, B=0,C=1,D=1인 경우에 출력 Y가 1이 된다.

entity MUX_GATE is --MUX_GATE entity 선언

port(a, b, c: in bit; sel : in bit_vector(1 downto 0); --입출력 선언

Y : out bit);

end;

architecture with_select of MUX_GATE is --architecture에서 내부회로 서술

begin

with sel select

Y <= (a or b) when "00",--sel 0이면 a or b

(b and c) when "01", -- sel 1이면 b or c

a when others;

end;

entity tb_MUX_GATE is --tb entity 선언

end tb_MUX_GATE ;

architecture simulation of tb_MUX_GATE is --tb achitecture 선언

component MUX_GATE --component 선언

port (a, b, c: in bit; sel : in bit_vector(1 downto 0);

Y : out bit);

end component;

signal a,b,c,d : bit; signal sel : bit_vector(1 downto 0);

begin

A <= '0', '1' after 10 ns, '0' after 20 ns, '1' after 30 ns, '0' after 40 ns; --파형 생성문으로 입력 신호 생성


B <= '0', '1' after 15 ns, '0' after 25 ns, '1' after 35 ns, '0' after 45 ns;

C <= '0', '1' after 20 ns, '0' after 30 ns, '1' after 40 ns, '0' after 50 ns;

SEL <= "00", "01" after 20 ns, "00" after 40 ns, "01" after 60 ns, "00" after 80 ns;

U0 : MUX_GATE port map (A=>A,B=>B,C=>C, SEL=> SEL, Y=>open); --component 실제화

end ;

 

3번

```
entity comparator is --comparator entity 선언
port(A, B: in bit; Equal,BigA,BigB : out bit); --입출력 선언
end comparator;
```

architecture behavioral of comparator is --아키텍처 선언

```
begin
process (A, B) --process문(A또는B가 바뀌면 동작)
begin
Equal<='0'; BigA<='0'; BigB<='0'; -- 기본값 0
if (A = B) then Equal<='1';-- A=B이면 Equal=1
elsif (A>B) then BigA<='1';-- A>B이면 BigA=1
else BigB<='1'; -- A<B이면 BigB=1
end if;
end process;
end;
```

```
entity tb_comparator is --tb_comparator 선언
end tb_comparator ;
```

architecture simulation of tb_comparator is --tb_architecture 선언

component comparator --component 선언

```
port (A, B: in bit; Equal,BigA,BigB : out bit);
end component;
```


signal signal_a,signal_b : bit; --signal선언

begin

signal_a <= '0', '1' after 20 ns, '0' after 40 ns; --파형 생성문으로 입력 신호 생성

signal_b <= '0', '1' after 10 ns, '0' after 20 ns, '1' after 30 ns, '0' after 40 ns;

```
U0 : comparator port map (A=>signal_a, B=>signal_b, Equal=>open,BigA=>open,BigB=>open); --component 실체화
end;
```

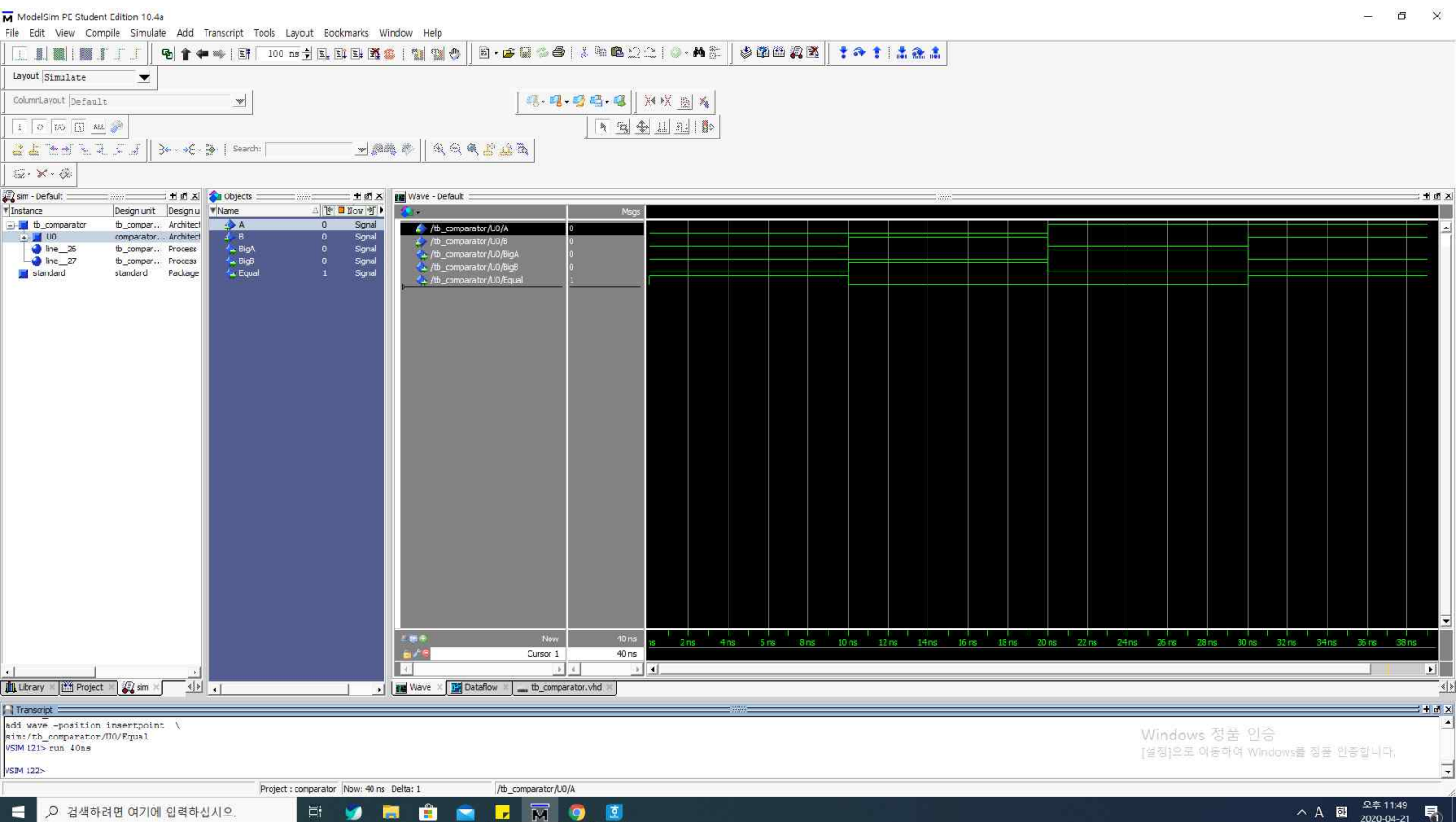

오후 11:47

4번

```
entity dff_gate is -- entity 선언
port ( a,b,c,d : in bit; q : out bit; -- 입출력
      clk : in bit);
end dff_gate;

architecture behavioral of dff_gate is -- 아키텍처 선언
signal K,L,N,P : bit; -- 신호 선언
begin
process (clk) -- 프로세스문 clk이 바뀌면 동작
begin

if (clk'event and clk = '1') then -- 라이징 클럭으로 바뀔 때
K <= (a or b); -- 연산
L <= (c nand d);
N<=L;
P <=(K nor N);
q <= P;
end if; -- if문 종료

end process; -- 프로세스문 종료
end behavioral; -- 아키텍처 종료

entity tb_dff_gate is -- 테스트벤치 선언
end tb_dff_gate ;

architecture simulation of tb_dff_gate is -- 테스트벤치 아키텍처
component dff_gate --컴포넌트 선언
port ( a,b,c,d : in bit; -- 입출력
      q : out bit;
      clk : in bit);
end component; -- 컴포넌트 종료

constant HALF_PERIOD_100M : time := 5 ns ; --클럭신호 주파수 200Mhz

signal a,b,c,d : bit; -- signal선언
signal clk : bit;

begin

clk_gen : process -- 프로세스문
begin

while (true) loop -- while loop
clk <= '0' ; wait for HALF_PERIOD_100M ;
clk <= '1' ; wait for HALF_PERIOD_100M ;
end loop; --while loop 종료

end process; -- 프로세스문 종료

a <= '0', '1' after 20 ns, '0' after 40 ns; --파형 생성문으로 입력 신호 생성
b <= '0', '1' after 10 ns, '0' after 20 ns, '1' after 30 ns, '0' after 40 ns;
c <= '0', '1' after 40 ns, '0' after 80 ns;
d <= '0', '1' after 20 ns, '0' after 40 ns, '1' after 60 ns, '0' after 80 ns;

u0: dff_gate port map (a=>a,b=>b,c=>c,d=>d, q => open, clk=>clk); -- 컴포넌트 실체화

end simulation; -- 종료
```

